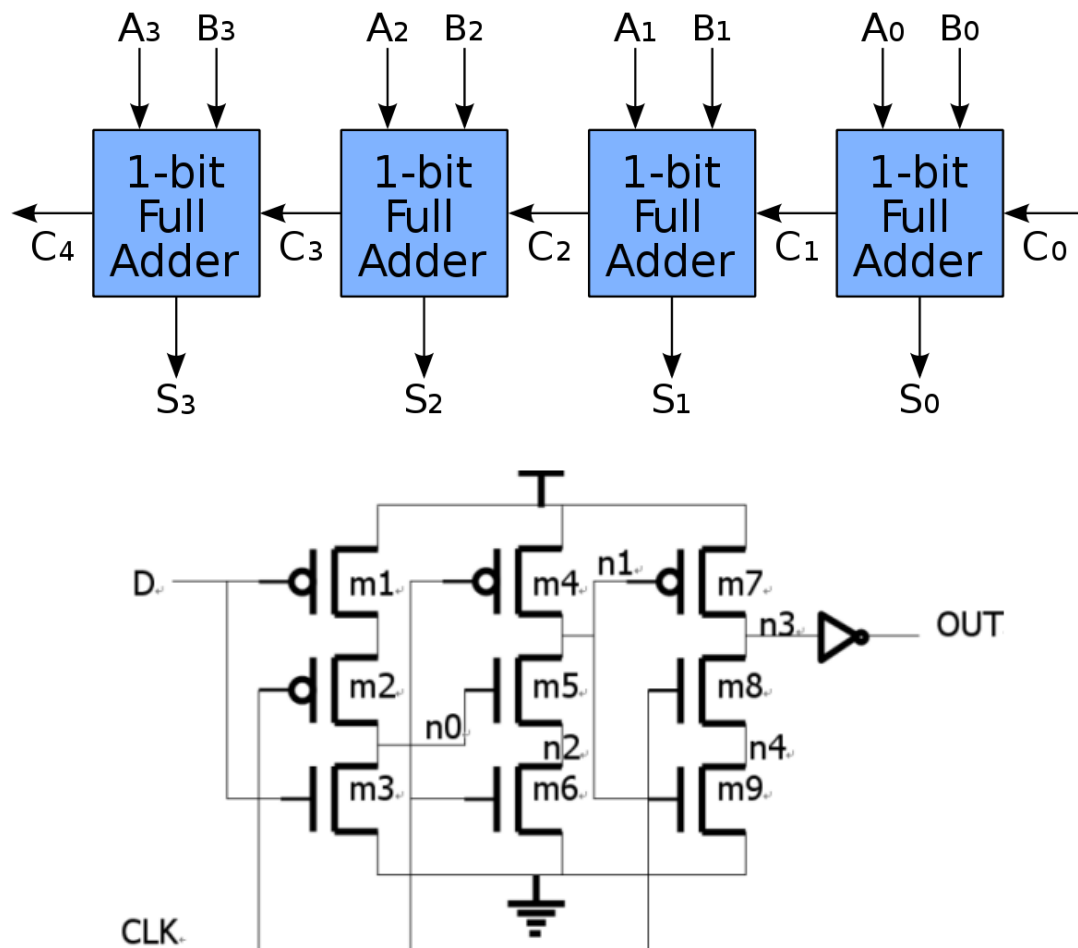


1. A 4-bit ripple adder as shown at Fig.1 is designed with Fully Complementary Static Logic Gate for FA. Input signals are $A[3:0]$, $B[3:0]$ and C_{in} which are provided by a unit size inverter. Outputs are $Sum[3:0]$ with loading of 5 unit size inverters connected in parallelism (FO5). You shall provide SPICE simulation results of timing and power waveforms.

- (1) Try your best to design the fastest adder. First, show your block diagrams in terms of the 1-bit Full-Adder(FA). Second, show the circuit schematic of each block. Use logic effort concepts (you do not have to write down the procedure) to design transistor widths. Describe your design concept. (40%)


下圖是 4-bit ripple adder 的 block diagram，其中 A、B、C 皆有通過 INV 以及 DFF 才接到 FULL ADDER 的輸入，輸出也有接上 DFF。




我根據講義對於此電路的分析來 sizing 此 DFF 的 transistor，而最後的 size 如下表。

	M1	M2	M3	M4	M5	M6	M7	M8	M9	INVp	INVn
nfin	4	4	2	4	2	2	4	2	2	2	1

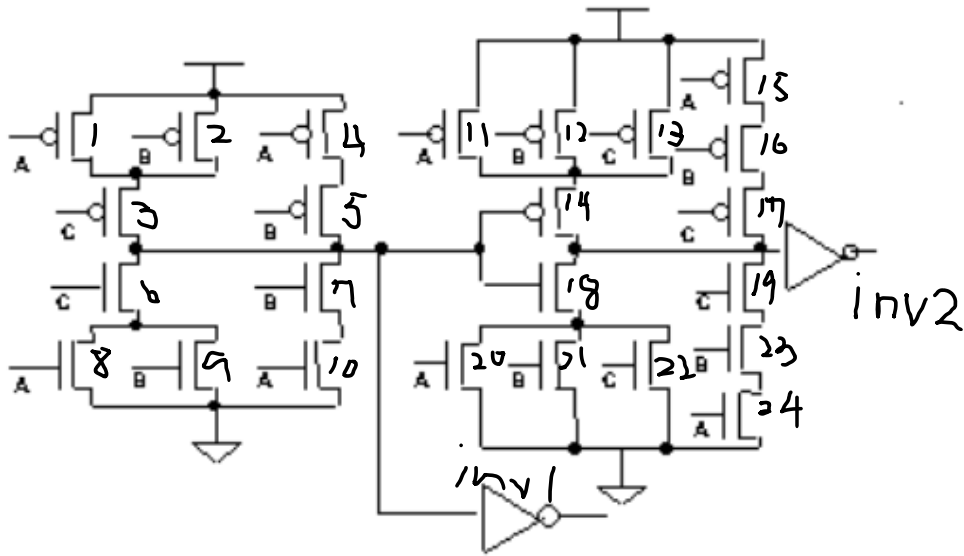而下圖是 1-bit Full Adder 的 Schematic，電晶體的編號會在 SIZING 的時候使用到



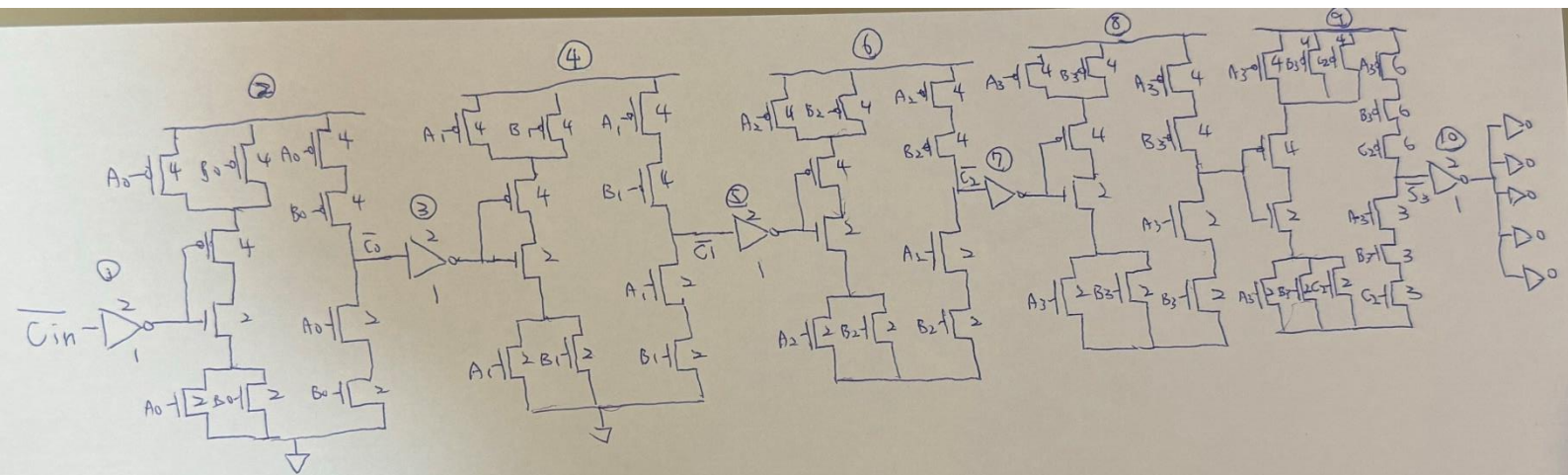題目要求我們使用 logic effort concept 來 sizing 電晶體，因此我打算分析最長的那條 critical path，也就是 Cin 到 S3 的路徑，而下圖是這條路徑的架構圖。



而我們可以將電路分級來計算 logic effort，因題目說無須列出過程，則以下省略。

Level	1	2	3	4	5	6	7	8	9	10
g	3/3	4/3	3/3	6/3	3/3	6/3	3/3	6/3	9/3	3/3
P	3/3	12/3	3/3	12/3	3/3	12/3	3/3	12/3	15/3	3/3

透過計算 logic effort，並考慮 SUM 的每個 bit 都有接一組 FO5 的情況下，我會將四組 FULL ADDER 分開 SIZING，並且會越來越大。

第一級 full adder

	1	2	3	4	5	6	7	8	9	10	11	12	13	14
nfin	1	1	1	1	1	7	7	7	7	7	5	5	5	5
	15	16	17	18	19	20	21	22	23	24	Inv1p	Inv1n	Inv2p	Inv2n
nfin	5	5	5	3	3	3	3	3	3	3	2	1	2	1

第二級 full adder

	1	2	3	4	5	6	7	8	9	10	11	12	13	14
nfin	1	1	1	1	1	8	8	8	8	8	6	6	6	6
	15	16	17	18	19	20	21	22	23	24	Inv1p	Inv1n	Inv2p	Inv2n
nfin	6	6	6	4	4	4	4	4	4	4	2	1	2	1


第三級 full adder

	1	2	3	4	5	6	7	8	9	10	11	12	13	14
nfin	1	1	1	1	1	9	9	9	9	9	7	7	7	7
	15	16	17	18	19	20	21	22	23	24	Inv1p	Inv1n	Inv2p	Inv2n
nfin	7	7	7	5	5	5	5	5	5	5	2	1	2	1

第四級 full adder

	1	2	3	4	5	6	7	8	9	10	11	12	13	14
nfin	1	1	1	1	1	10	10	10	10	10	8	8	8	8
	15	16	17	18	19	20	21	22	23	24	Inv1p	Inv1n	Inv2p	Inv2n
nfin	8	8	8	6	6	6	6	6	6	6	2	1	2	1

 
(2) Based on the design of (1), run SPICE to find the the propagation delay time (with pattern from 000011110 to 000011111 (A[3:0]@B[3:0]@Cin). Determine the maximum propagation of a clock with the delay time estimated by SPICE. (20%)
 tpd 為經過 DFF 後的 Cin=0.5VDD 到 critical path 輸出=0.5VDD 的所花的時間，因此我在模擬時將 Cin 從 0 變成 VDD，並觀察波型，由下圖可看出 tpd=63ps。



而透過 meas 指令，可得出精確的 tpd=63.4306ps。


```
***** transient analysis tnom= 25.000 temp= 25.000 *****
tpd= 63.4306p targ= 330.4724p trig= 267.0418p
```

 propagation delay time 為86.8991ps(worst case)，因 t_r 和 t_f 皆為 20ps，因此將 clock period 設為 104ps，但經過模擬後發現這樣電路無法正常運作，而之後我透過 spice 模擬發現當 clock period=165ps 時，電路能正常運作，因此 max clock frequency=6.06GHz。



(3) Run SPICE to get the average, peak and leakage power dissipation and energy/bit, respectively of this adder with loading (FO4) when working at the maximum working frequency. (20%)

下圖是有包含 power 的波形。

 

我們可以使用 meas 指令來計算 average power 及 peak power。

```
avgpower= 135.6107u from= 0. to= 5.0000n
peakpower= 940.0539u at= 15.6062p
           from= 0. to= 5.0000n
```

之後再將 input 電壓皆設為 0 來計算 leakage power 。

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
leakagepower= 10.5518u from= 0. to= 5.0000n

***** job concluded
```


接下來要計算 Energy/bit ， maximum working frequency=6.06GHz 。

$Average\ power/frequency=2.238*10^{-14}$


$Energy/bit=2.238*10^{-14}/4=0.56*10^{-14}J/bit=5.6fJ/bit$ 。

Average power	Peak power	Leakage power	Energy/bit
135.6107 μW	940.0539 μW	10.5518 μW	5.6fJ/bit

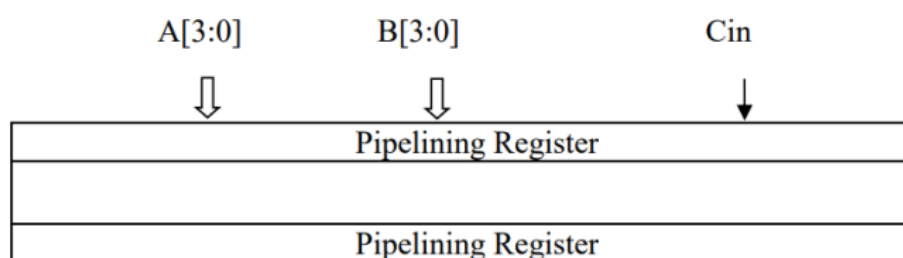
(4) Add one pipelining stage using the designed D register into the 4-bit ripple adder as shown at Fig.1(b). Run SPICE to find the the propagation delay time (with pattern from 000011110 to 000011111 (A[3:0]@B[3:0]@Cin) between pipelining stages to determine the maximum working frequency of the clock with the delay time estimated by SPICE. (20%)



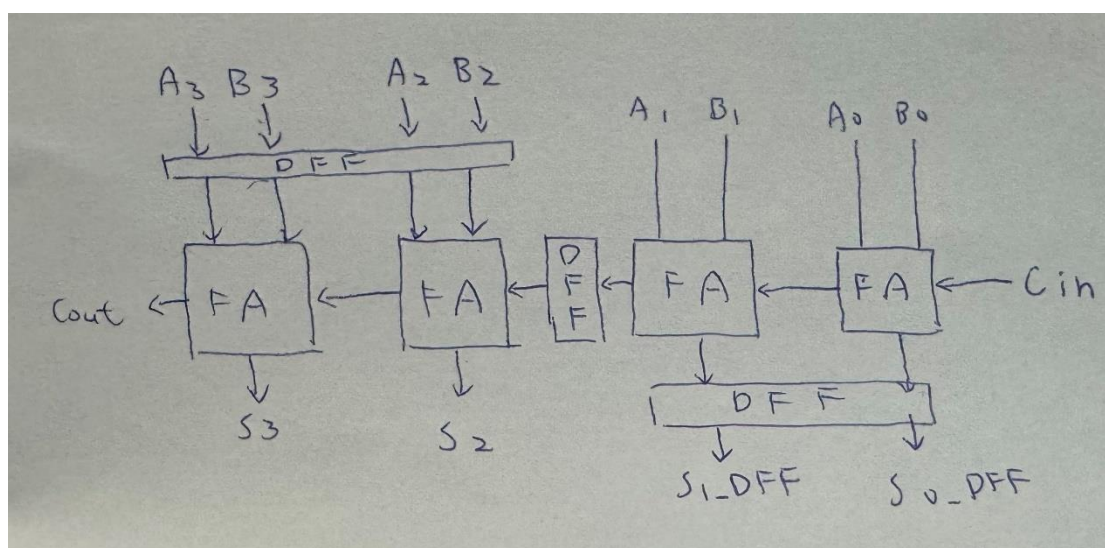下圖是我將電路加上 pipeline register 後的 block diagram ，其中 A 、 B 、 C 皆有通過 DFF 以及 INV ，且 S0_DFF 、 S1_DFF 、 S2 、 S3 也都有接 DFF 。



 因為加了 pipeline register，因此新的 critical path 變成 Cin 經過 DFF 後到 S1，而從下方波型可看出 $tpd=40ps$ 。



而我透過 meas 指令計算出精確的 $tpd=39.77ps$ 。

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
tpd= 39.7700p targ= 306.8090p trig= 267.0390p

***** job concluded
*****
```

我先將 clock period 用 80ps 代入，發現電路無法正常工作，而經過我的模擬發現，clock working frequency=10GHz(period=100ps)時，電路才能正常運作，波型如下圖。

